

①

# ADVD ASSIGNMENT

## MICROWIND

<u>Name</u>	<u>ID'S</u>
Harsh Agrawal	2019B2A30996P
Naman Mhata	2019B2A80981P
Kapil Nair	2019B4A30654P



②

# Problem Statement:- Design of an inverter


Design a CMOS inverter at 500 MHz with load capacitance of 10 pF.

- \* Use of CMOS to get highest output voltage swing compared to any other design style.

Schematic:-

Representation Purpose only.

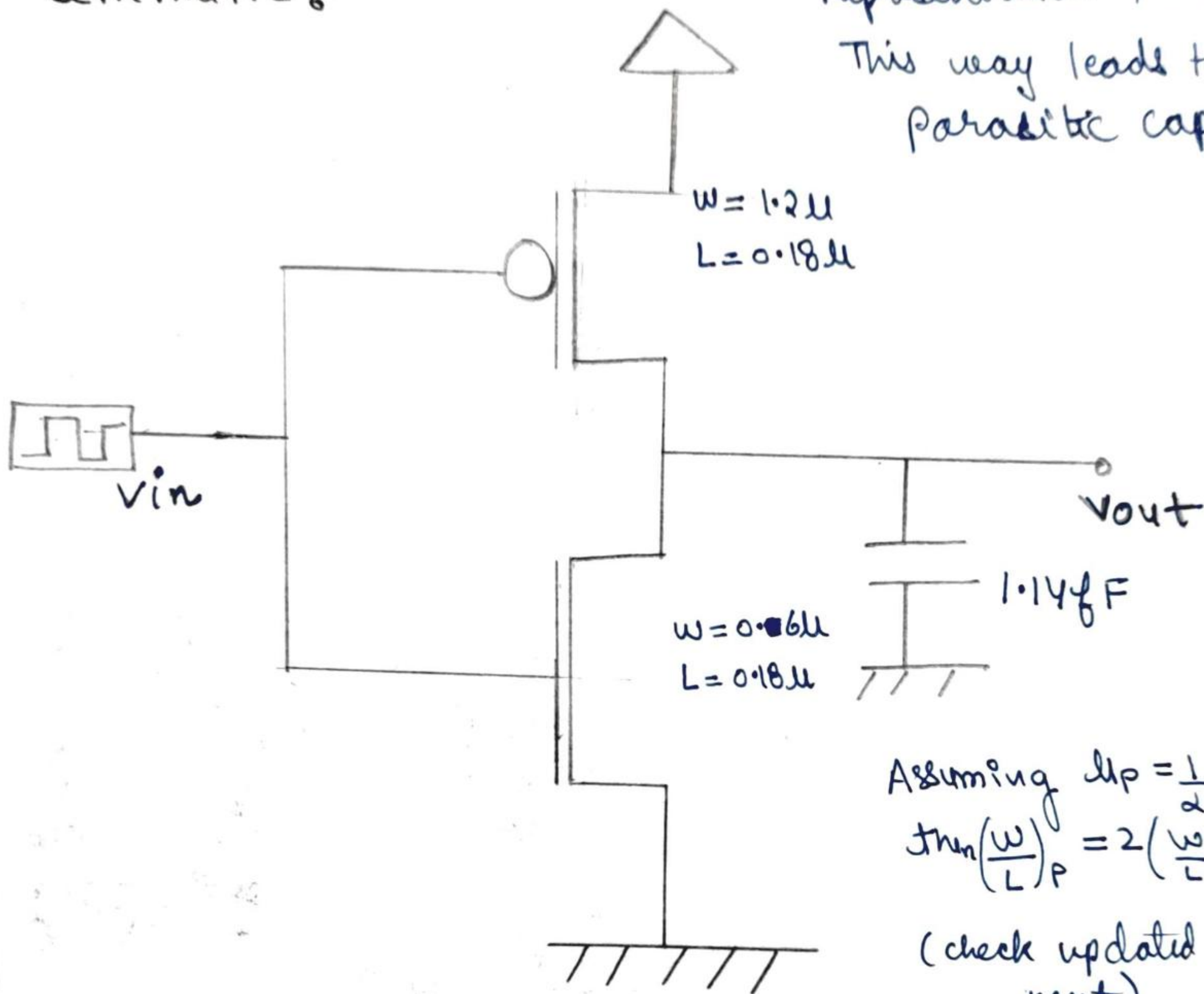
This way leads to more parasitic capacitance.



$$\text{Assuming } \mu_p = \frac{1}{2} \mu_n,$$

$$th_n\left(\frac{W}{L}\right)_p = 2\left(\frac{W}{L}\right)_n$$

(check updated values next)

 

Actual layout implementation



(3)

DATE \_\_\_\_\_

PAGE \_\_\_\_\_

### Determining $W_p, W_n$ :-

when observing the outputs of delay graph ( $t_{out}$ ) based on the assumption of  $\frac{W_n}{W_p} = 2$ , the  $T_{PLH} = 10$  pS,

and  $T_{PHL} = 15$  pS, i.e.  $T_{PLH} \neq T_{PHL}$ .

It is known that the maximum current drive is at  $V_M = V_{th}$  (switching threshold) which is  $V_{DD}$  for our chosen design. To achieve that, one condition must satisfy:  $T_{PHL} = T_{PLH}$  (i.e. equal current drive).

\* Varying  $W_p/W_n$ , keeping either constant, after various iterations, the required  $W_p/W_n$  came out to be 1.3 for  $W_p/W_n$  equal.

\* For this design, given  $L = 180$  nm,  $W_n = 0.600$   $\mu$ m that is  $W_p = 0.780$   $\mu$ m

\* Finally,  $T_{PHL} = T_{PLH} = 10$  pS (although due to some problems with microwind software, exact,  $L, W_p, W_n$  values could not be set).

$$\Rightarrow \left(\frac{W}{L}\right)_n = 3.33, \left(\frac{W}{L}\right)_p = 4.33, \frac{W_p}{W_n} = 1.3$$


\* for  $\frac{W_p}{W_n} > 1.3$ , PMOS drives more current (higher  $T_{PLH}$ )

\* for  $\frac{W_p}{W_n} < 1.3$ , NMOS drives more current (lower  $T_{PLH}$ )



4



Layout:-

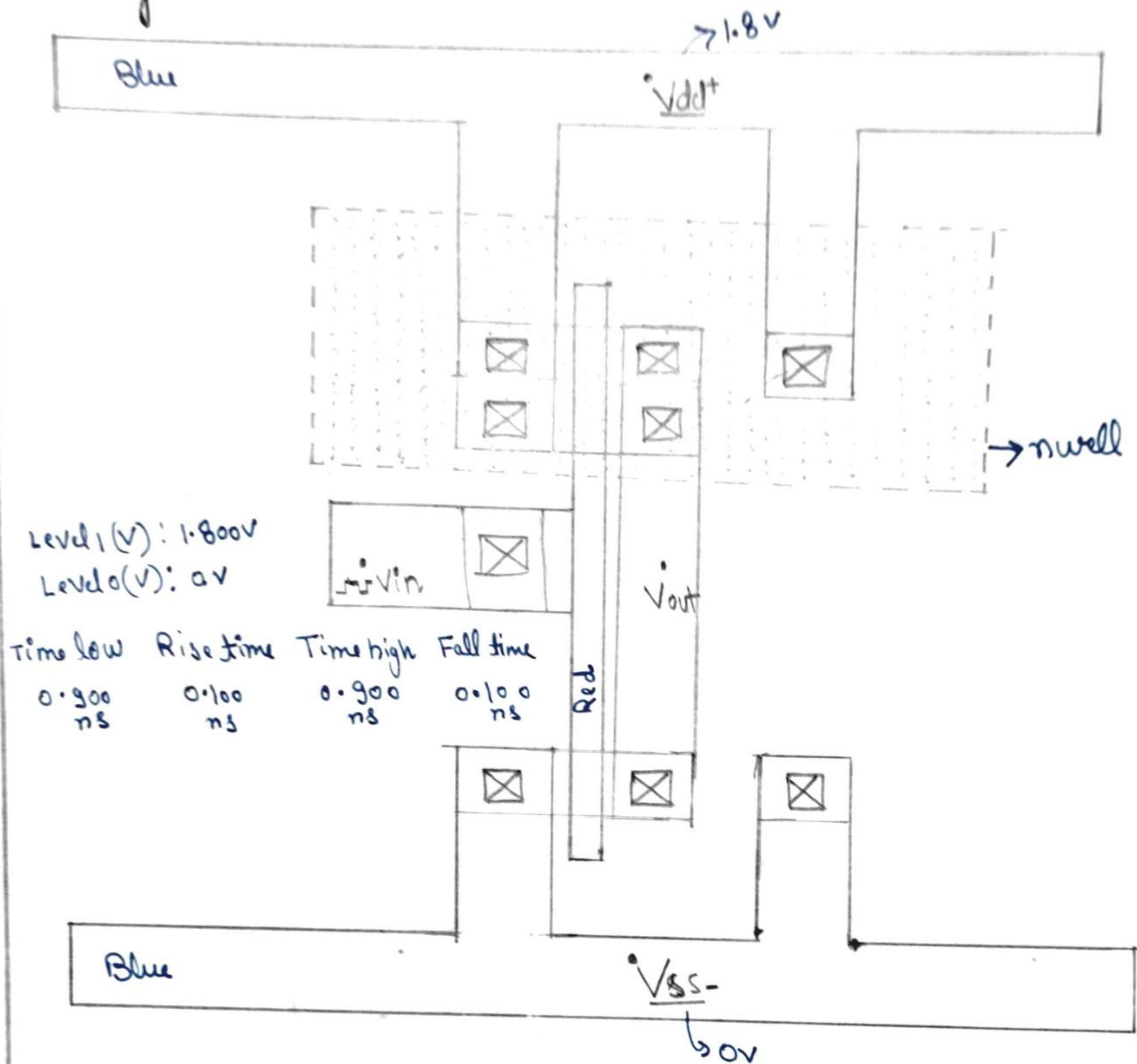

- ① DRC is checked using microwind, which gives no errors.
- ② PEK extraction (Microwind)  $\Rightarrow$  final output capacitance = 1.93 fF (0.0193 % of given 10 pF)
- ③ DSCH was used to draw schematic and Microwind for layout. Both of them match and LVS is passed.

(5)



Inverter output with 1 pf load:-

  

Remarks:- Not a feasible design.




6

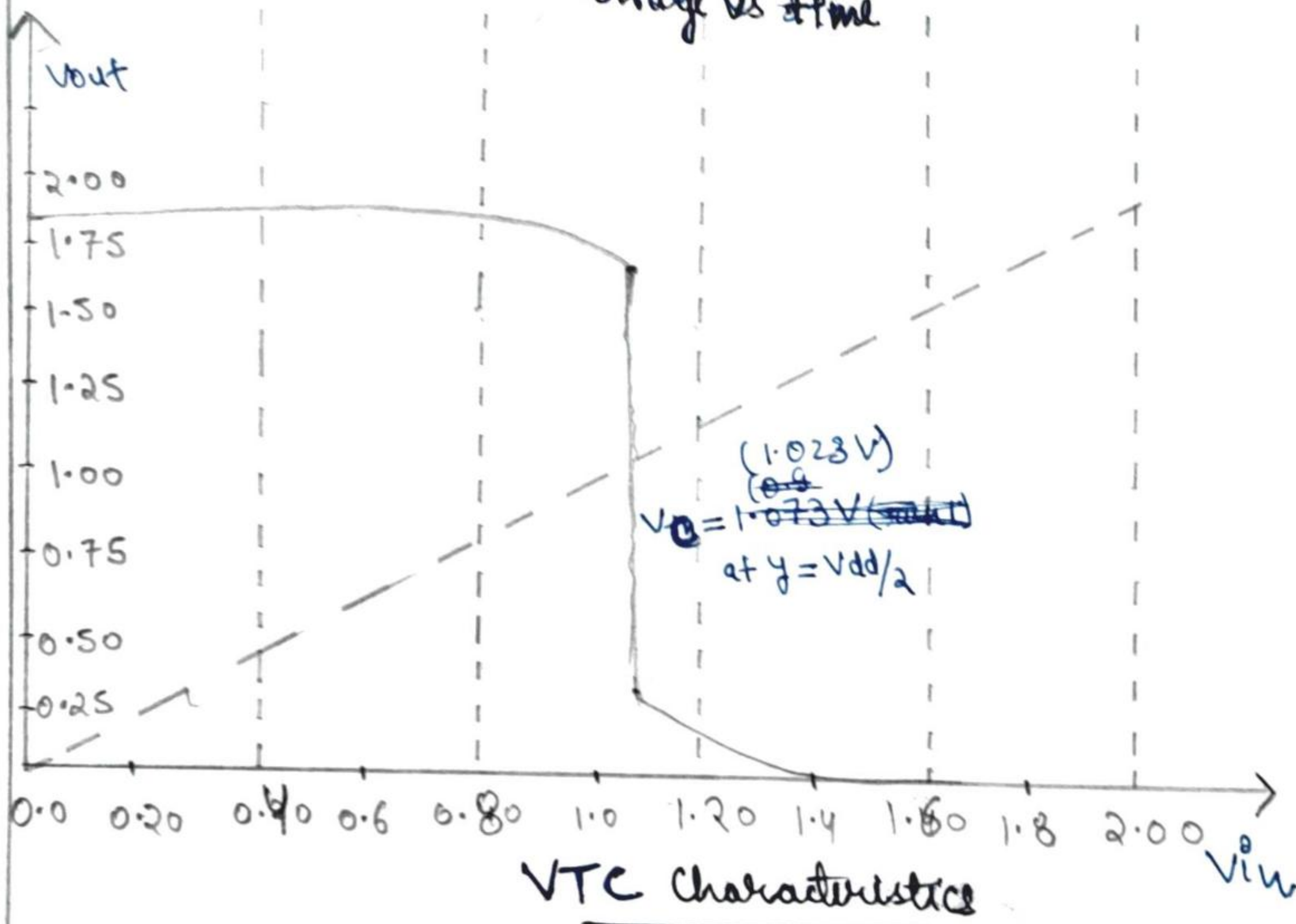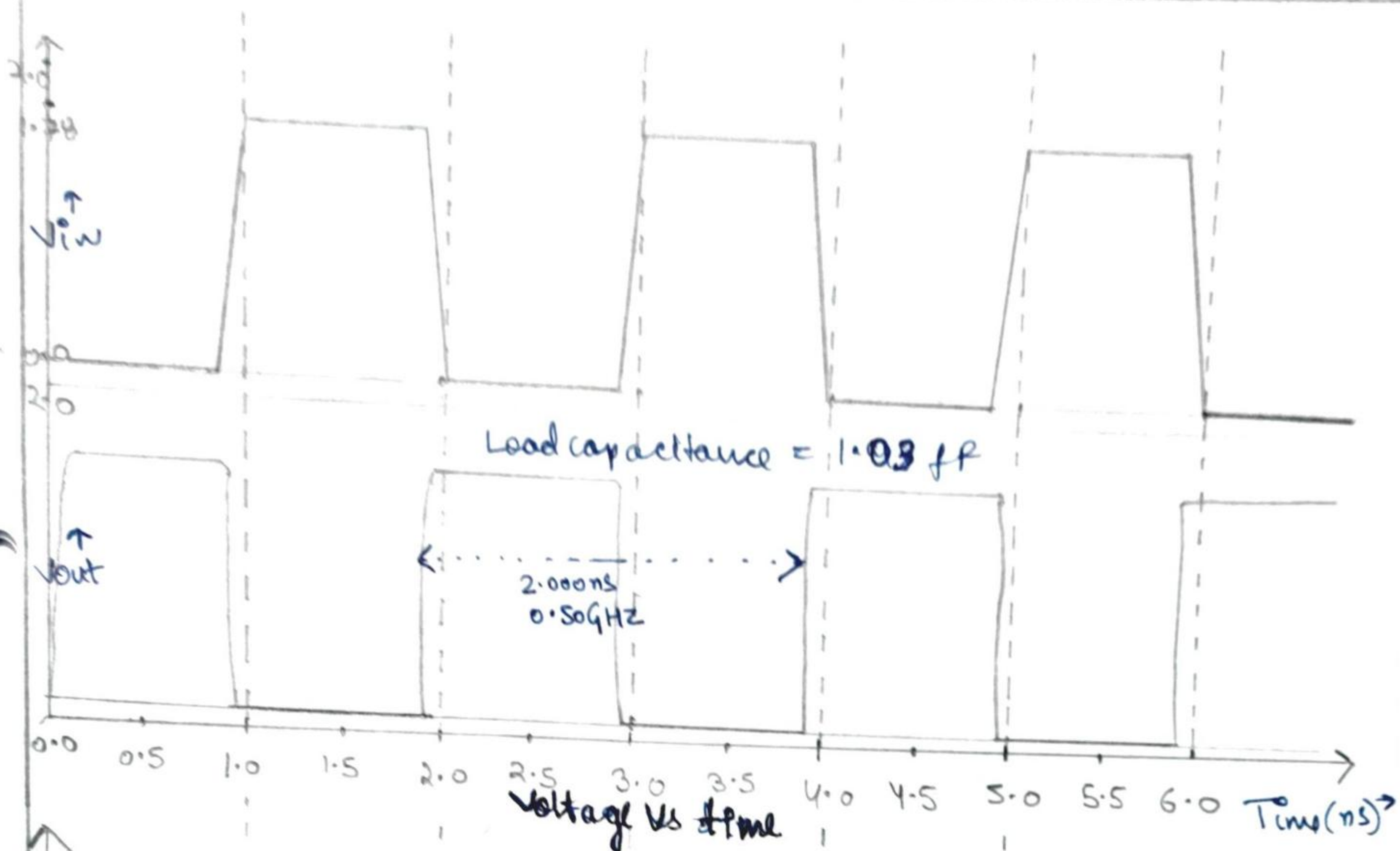

⑦

# Voltages and currents :-

 



Calculations:- (8)



DATE \_\_\_\_\_

PAGE \_\_\_\_\_

$$C_g = 2.18 \text{ fF} \quad C_L = 1.03 \text{ fF}, \quad V_{DD} = 1.8 \text{ V}, \quad f = 500 \text{ MHz (of operation)}$$
$$\text{Switching power for a cycle} = C_L V_{DD}^2$$

$$\begin{aligned} \text{Switching power per unit time} &= C_L V_{DD}^2 f \\ &= (1.03 \times 10^{-15} \times (1.8)^2 \times 5 \times 10^8) \text{ W} \\ &= 1.6686 \text{ }\mu\text{W} \end{aligned}$$

$$\text{Dynamic power (by Mcrowind)} = 4.039 \text{ }\mu\text{W}$$



$$\begin{aligned} \text{Short circuit power} &= \text{Dynamic power} - \text{Switching power} \\ &= 2.3704 \text{ }\mu\text{W} \end{aligned}$$

$$\begin{aligned} \text{Expected dynamic power consumption (1st order equations)} &= C_g V_{DD}^2 f \\ &= 2.18 \times 10^{-15} \times (1.8)^2 \times 5 \times 10^8 \\ &= 3.53 \text{ }\mu\text{W} \end{aligned}$$

$$\begin{aligned} \text{Switching power at an instant} &= C_L \times V_{DD} \times V_{out} \times f \\ \text{Short circuit power} &= I_{DS} \times V_{DD} \end{aligned}$$




9

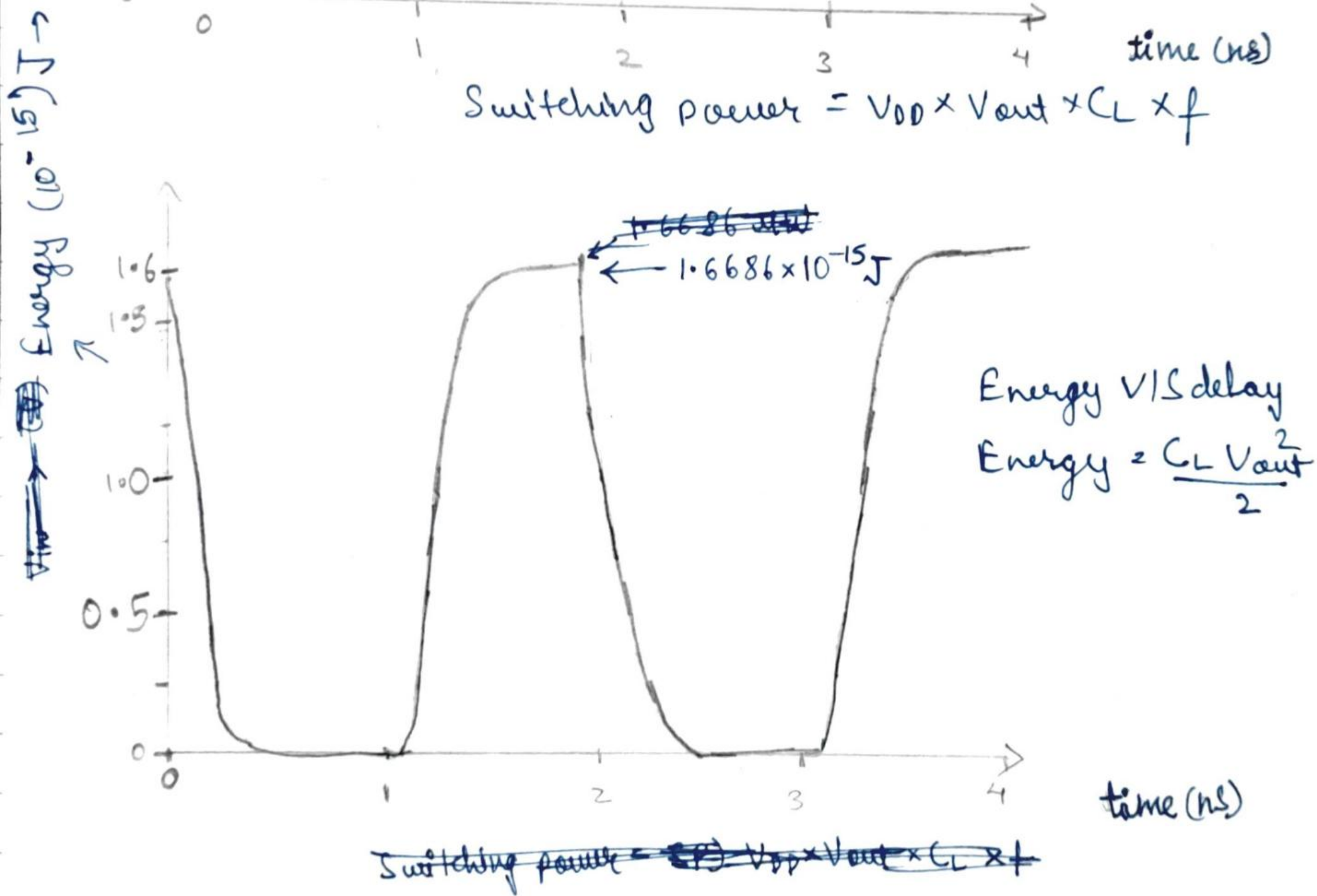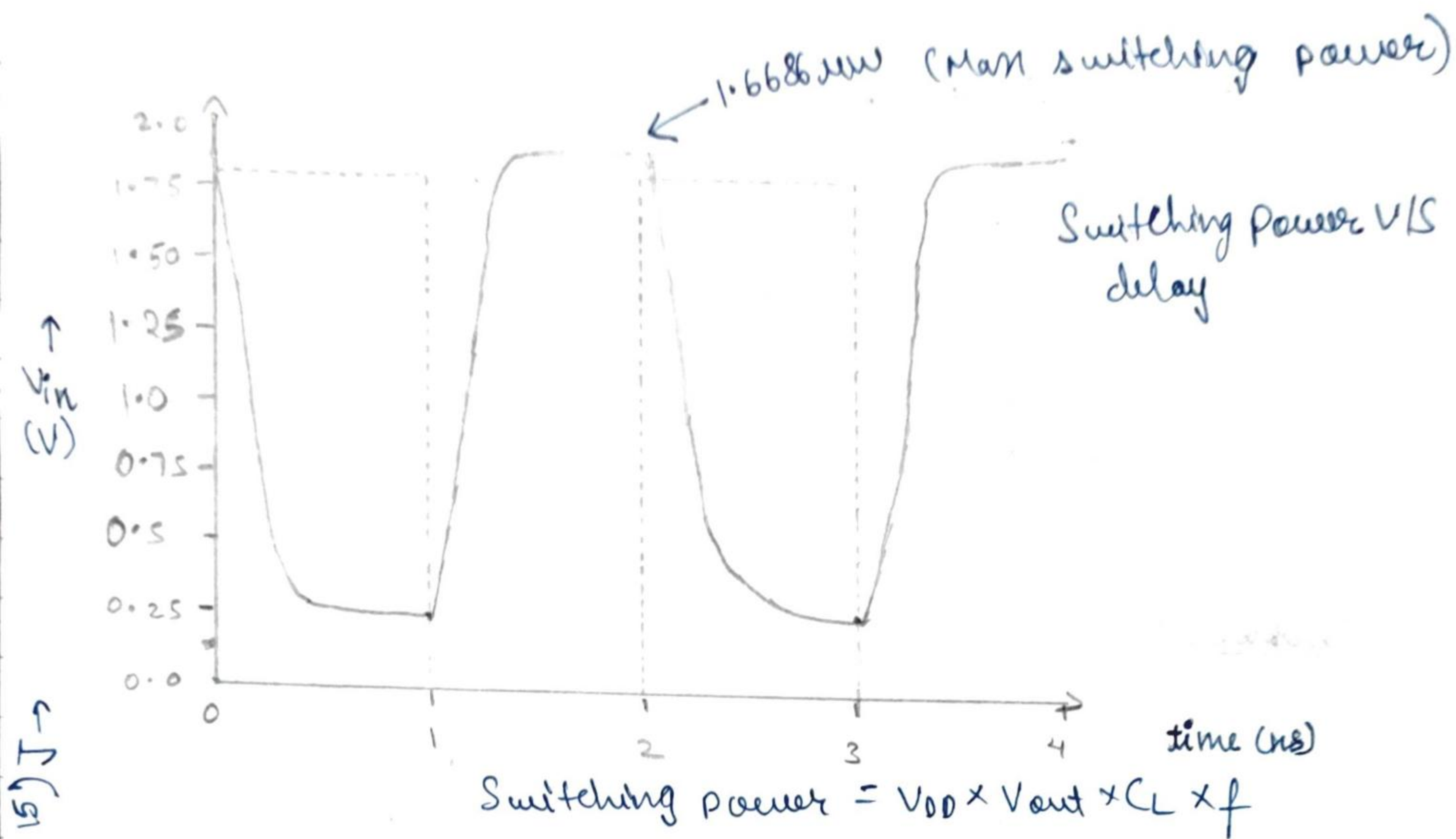



Short Circuit Power ( $\mu W$ )

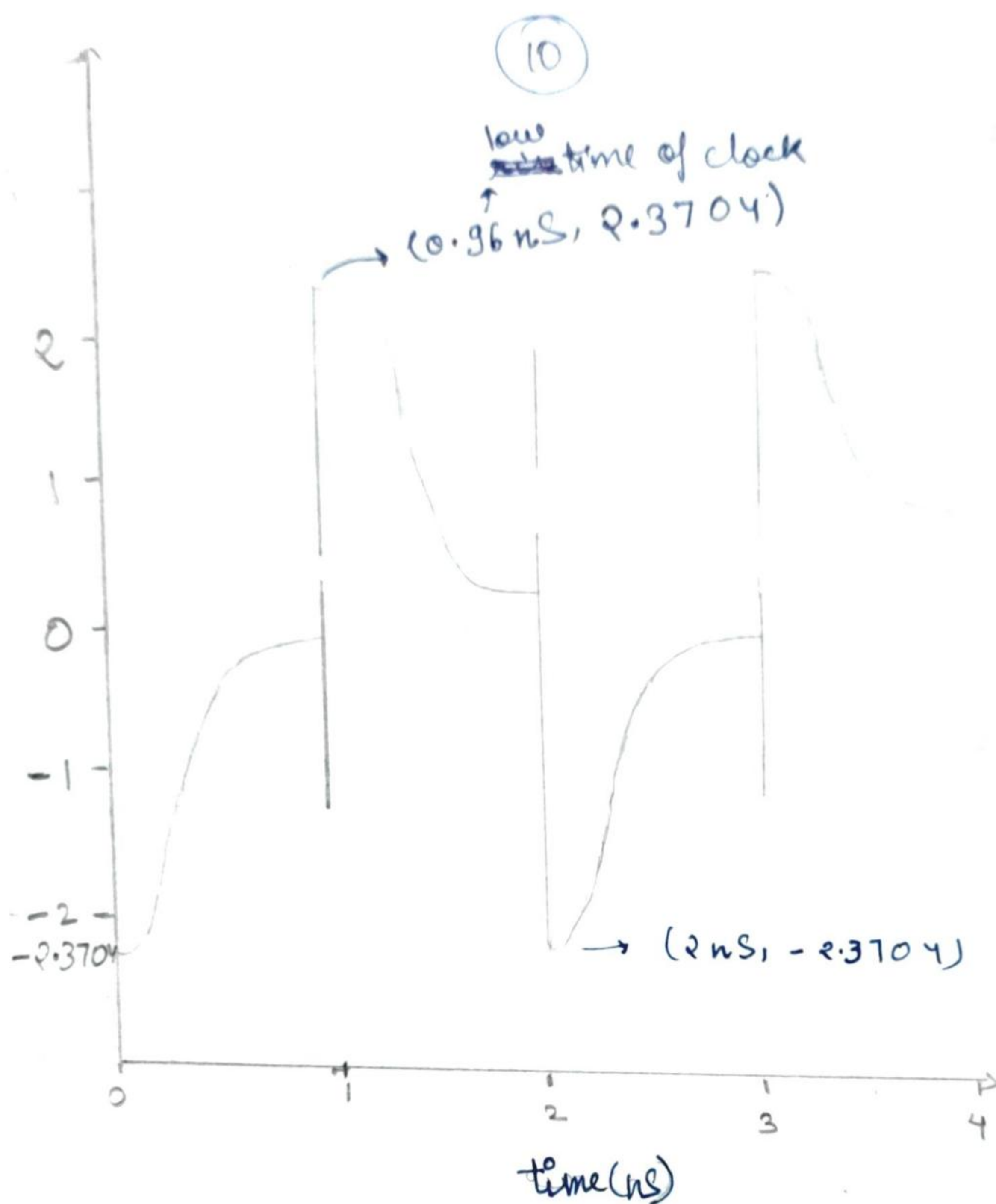



## Results and Conclusions :-

The designed inverter works for frequencies beyond 500MHz, but for observation purposes, operated at 500MHz


L = 180 nm	Dynamic power = 4.039 $\mu$ W
Wn = 0.60 $\mu$ m	<del>Static</del> Short ckt power = 2.3704 $\mu$ W
wp = 0.78 $\mu$ m	Switching power = 1.6686 $\mu$ W

## Problems

- i) Load capacitance of 10 pF is not possible (rather not desired) as asked in the question, for a small digital circuit like an inverter. [consider page (5) for sample]
- ii) Microwind kept setting the length to 200 nm in contrast to 180 nm (desired input)
- iii) Energy, static and switching power could not be visualized in Microwind.



5 lambda  
0.500μm

 



5 lambda  
0.500µm



Navigator

Props | Device | Op

Node "Vout" ...

Property: variable

☒ Appear in simu

1.03 fF

68 ohm

6 µm


0.00 nH

Vout, visible ,  
---Node Properties---  
CAPA:(1.03fF)  
.Metal Capa:0.71 fF  
.Crosstalk :0.00 fF  
.Diffusion :0.32 fF  
.Gate :0.00 fF


Hide

Unselect



 



 





Navigator



Props

Device

Op



Node "Vin"



Property: clock



Appear in simu



2.18 fF



101 ohm



9  $\mu\text{m}$



0.01 nH

Ca

Vin, visible , clock

---Node Properties---

CAPA:(2.18fF)

.Metal Capa:0.21 fF

.Crosstalk :0.00 fF

.Diffusion :0.00 fF

.Gate :1.97 fF



Hide

Unselect